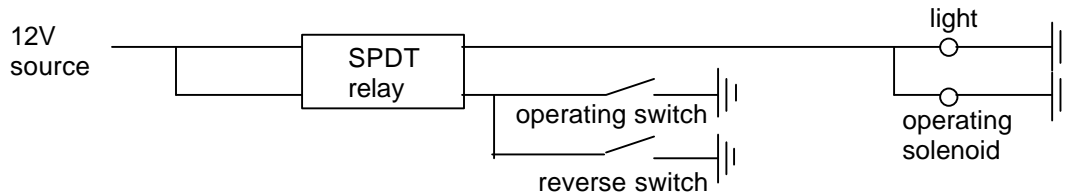


## Overdrive Wiring

This wiring schematic will permit overdrive to be selected in any gear except reverse. When switched on, the overdrive will operate continuously during shifts between the forward gears.



The SPDT relay is wired to power to the solenoid when the relay is not energized, i.e. it is connected to the normally closed contact. The overdrive will operate when both the operating switch and reverse switch are off. I would recommend a fuse and indicator light with this set up.